

CMP1202: ELECTRONICS II

CAT#1

DATE: March 27, 2019

DURATION: 1 HOUR

SOLUTIONS

NAME: _____

REGISTRATION NUMBER: _____

STUDENT NUMBER: _____

PROGRAMME (BSc.CMP I, II, E.T.C.): _____

SIGNATURE: _____

SOLUTIONS

1 **C**

2 **A**

3 **C**

4 **B**

5 **B**

6 **A**

7 **A**

8 **C**

9 **D**

10 **A**

CMP1202: ELECTRONICS II

CAT#1

DATE: March 27, 2019

DURATION: 1 HOUR

Instructions: This paper consists of objective type questions. Write down the correct options for each question on the answer sheet provided. Write clearly. Marks will be deducted for poorly presented work.

Constants: Thermal voltage $V_T = 25 \text{ mV}$,

$$V_{BE} = 0.7 \text{ V}$$

$$V_{CEsat} = 0.2 \text{ V}$$

- 1) The following are properties of an ideal operational amplifier except:
 - A) Infinite input impedance
 - B) Infinite bandwidth
 - C) Infinite closed loop gain
 - D) Zero output impedance
- 2) The purpose of frequency compensation in operational amplifier circuits is to ensure that they:
 - A) Are stable
 - B) Oscillate
 - C) Have an infinite bandwidth
 - D) Do not need input bias currents

Refer to Figure 1 for questions 3 – 5.

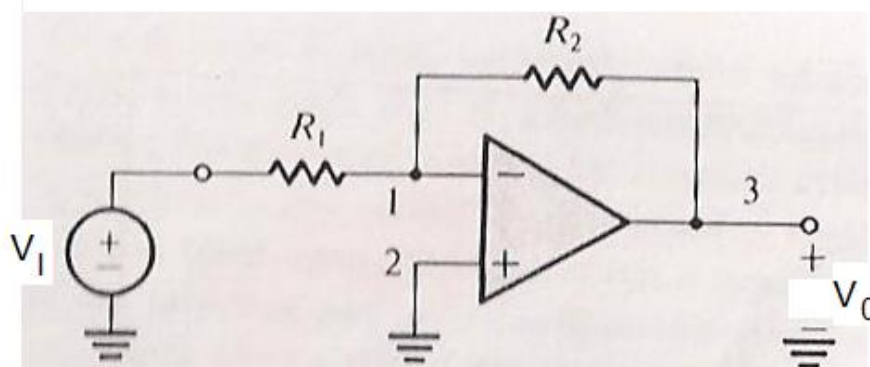


Figure 1

- 3) Using the circuit of Figure 1 and assuming an ideal operational amplifier, design an inverting amplifier with a voltage gain of 16.99 dB under the constraint of having to use resistors no larger than 10 M Ω .
 - A) $R_1 = 100 \text{ k}\Omega$, $R_2 = 5 \text{ M}\Omega$
 - B) $R_1 = 1 \text{ k}\Omega$, $R_2 = 7 \text{ M}\Omega$
 - C) $R_1 = 1.4 \text{ M}\Omega$, $R_2 = 10 \text{ M}\Omega$
 - D) $R_1 = 200 \text{ k}\Omega$, $R_2 = 10 \text{ M}\Omega$
- 4) What is the input resistance of your amplifier design in question 3?
 - A) 10 M Ω
 - B) 1.4 M Ω
 - C) 200 k Ω
 - D) 0
- 5) The circuit in Figure 1 can be converted into a miller integrator by replacing an element(s) as follows:

- A) R_1 with a capacitor
- C) R_1 and R_2 with capacitors

- B) R_2 with a capacitor
- D) R_2 with an inductor

6) A weighted summer circuit using an ideal operational amplifier has three inputs using $100\text{ k}\Omega$ resistors and a feedback resistor of $50\text{ k}\Omega$. A signal v_1 is connected to two of the inputs while a signal v_2 is connected to the third. If $v_1 = 3\text{ V}$ and $v_2 = -3\text{ V}$, what is v_o ?

- A) -1.5 V
- C) -6 V

- B) -4.5 V
- D) 1.5 V

7) One of the following statements is **TRUE**.

- A) In the saturation region β for a transistor drops drastically.
- C) A CE amplifier can only give unit voltage and current gains

- B) The transconductance of a BJT is explicitly determined by the dimensions of the device
- D) none

Refer to figure 2 for questions 8 - 10. Figure 2 shows a common emitter amplifier with d.c. collector current $I_c = 0.2\text{ mA}$, $\beta = 100$, $R_c = 47\text{ k}\Omega$, $R_s = 100\text{ k}\Omega$ and a large early voltage V_A . Assume that the bypass capacitor C_E has a large value and therefore at signal frequencies of interest it presents a very small impedance.

8) Obtain the voltage gain $A_v = V_o/V_s$.

- A) 376 V/V
- C) -41.8 V/V

- B) 32 V/V
- D) -46.4 V/V

9) Find the new voltage gain when the output of the amplifier is connected to a load resistor of $10\text{ k}\Omega$. (i.e. load resistor connected to collector)

- A) -6.6 V/V
- C) -8.14 V/V

- B) -42 V/V
- D) -7.33 V/V

10) The output resistance of the amplifier is:

- A) $47\text{ k}\Omega$
- C) $10\text{ k}\Omega$

- B) $8.25\text{ k}\Omega$
- D) none

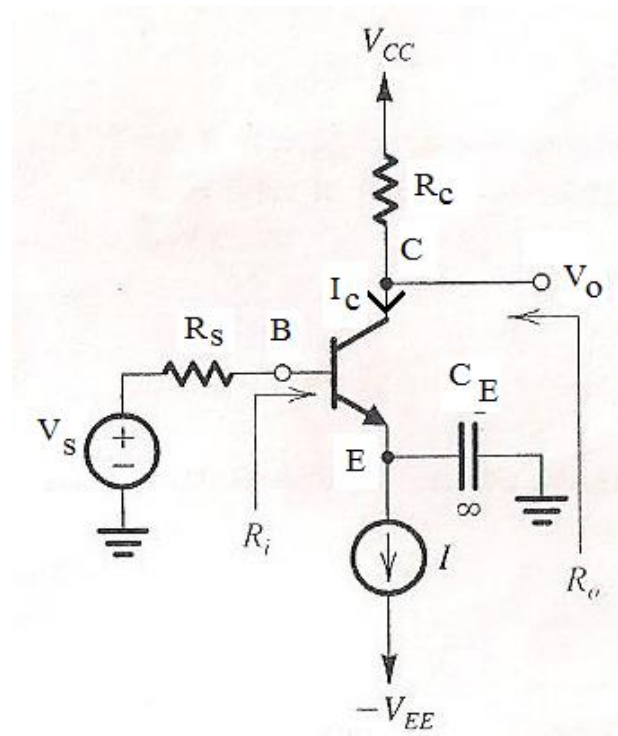


Figure 2

The End